
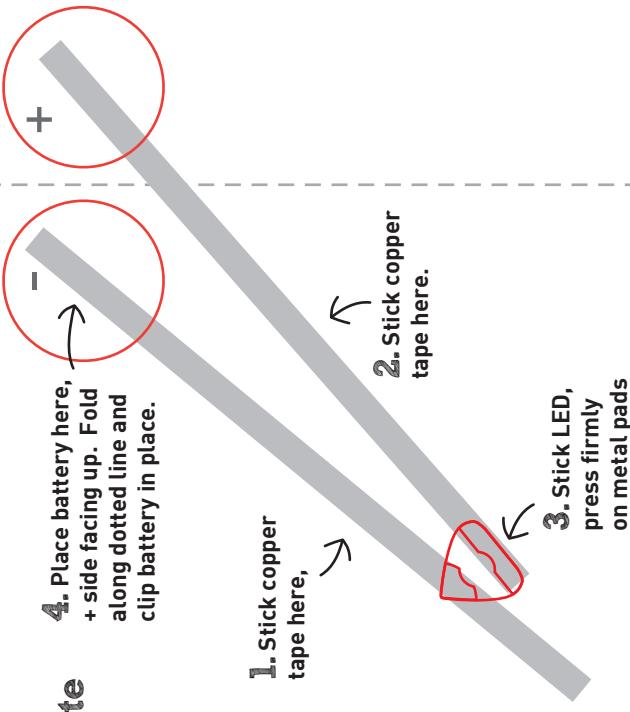


Circuit Template

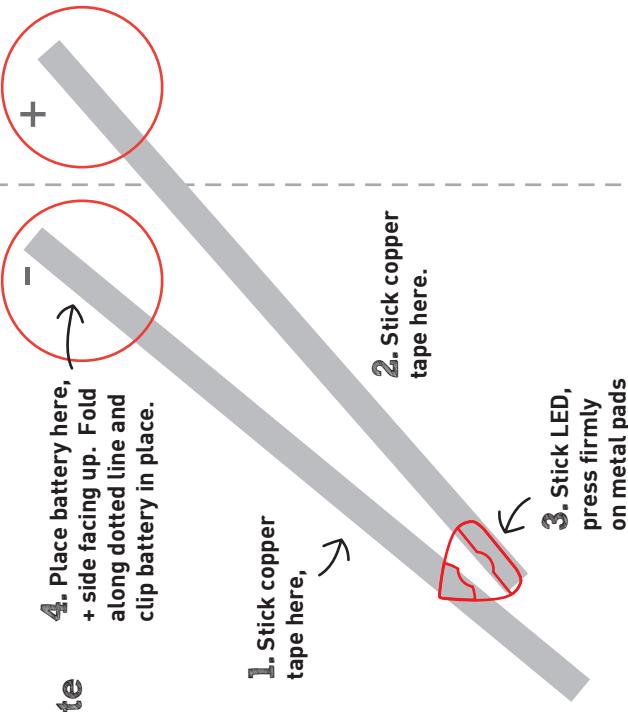

chibitronics.com

Circuit Template




chibitronics.com

Made with ❤ by:

Your Name

How does the circuit work?

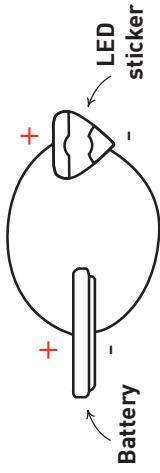When you connect the LED sticker to the battery in a complete loop with conductive tape like this:



power from the battery flows through the LED light, causing it to shine. This continuous loop is called a complete circuit.




Check out chibitronics.com for more circuit crafting projects!

Made with ❤ by:

Your Name

How does the circuit work?

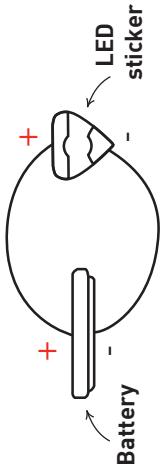When you connect the LED sticker to the battery in a complete loop with conductive tape like this:



power from the battery flows through the LED light, causing it to shine. This continuous loop is called a complete circuit.



Check out chibitronics.com for more circuit crafting projects!