

## Paper Circuit: Light-up Card

Made with ♥ by:

\_\_\_\_\_  
Your Name

← 5. Fold your card along this line and decorate. Congrats, your card is complete!



chibitronics.com

4. Place battery here, + side facing up. Fold along dotted line and clip battery in place.

1. Stick copper tape here,

2. Stick copper tape here.

3. Stick LED, press firmly on metal pads

## Paper Circuit: Light-up Card

Made with ♥ by:

\_\_\_\_\_  
Your Name

← 5. Fold your card along this line and decorate. Congrats, your card is complete!



chibitronics.com

4. Place battery here, + side facing up. Fold along dotted line and clip battery in place.

1. Stick copper tape here,

2. Stick copper tape here.

3. Stick LED, press firmly on metal pads