	I			
	Paper Circuit: Light-up Card	4. Place battery here, + side facing up. Fold along dotted line and	-	+
1	Made with ♥ by:	clip battery in place.		
ĺ				
	l 	1. Stick copper tape here,		
	Your Name	tape here,		
	 -		2. Stick copper	
	I		tape here.	
į	5. Fold your card along this	3. Stick LED,		
	line and decorate. Congrats,	press firmly		
	your card is complete!	on metal pads		
	(cc) (cc) Nor	is work is licensed under a Creative Commo nCommercial-ShareAlike 4.0 International ps://creativecommons.org/licenses/by-nc-sa	License:	
i	 			
	Paper Circuit:	4	_	+
	Light-up Card	4. Place battery here,+ side facing up. Fold	→	
į	Light up card	along dotted line and		
	I 	clip battery in place.		
	Made with 🎔 by:			[
į	1. Stick copper			
		tape here,		
	Your Name	Y	7	
	I		2. Stick copper	
i			tape here.	
	5. Fold your card along this			
i	line and decorate. Congrats,	3. Stick LED, press firmly		
	your card is complete!	on metal pads		
ĺ		his work is licensed under a Creative Comm	ions Attribution-	
į	This work is licensed under a Creative Commons Attribution-NonCommercial-ShareAlike 4.0 International License: https://creativecommons.org/licenses/by-nc-sa/4.0/			
	CHIDITIONICS.COM			

chibitronics.com