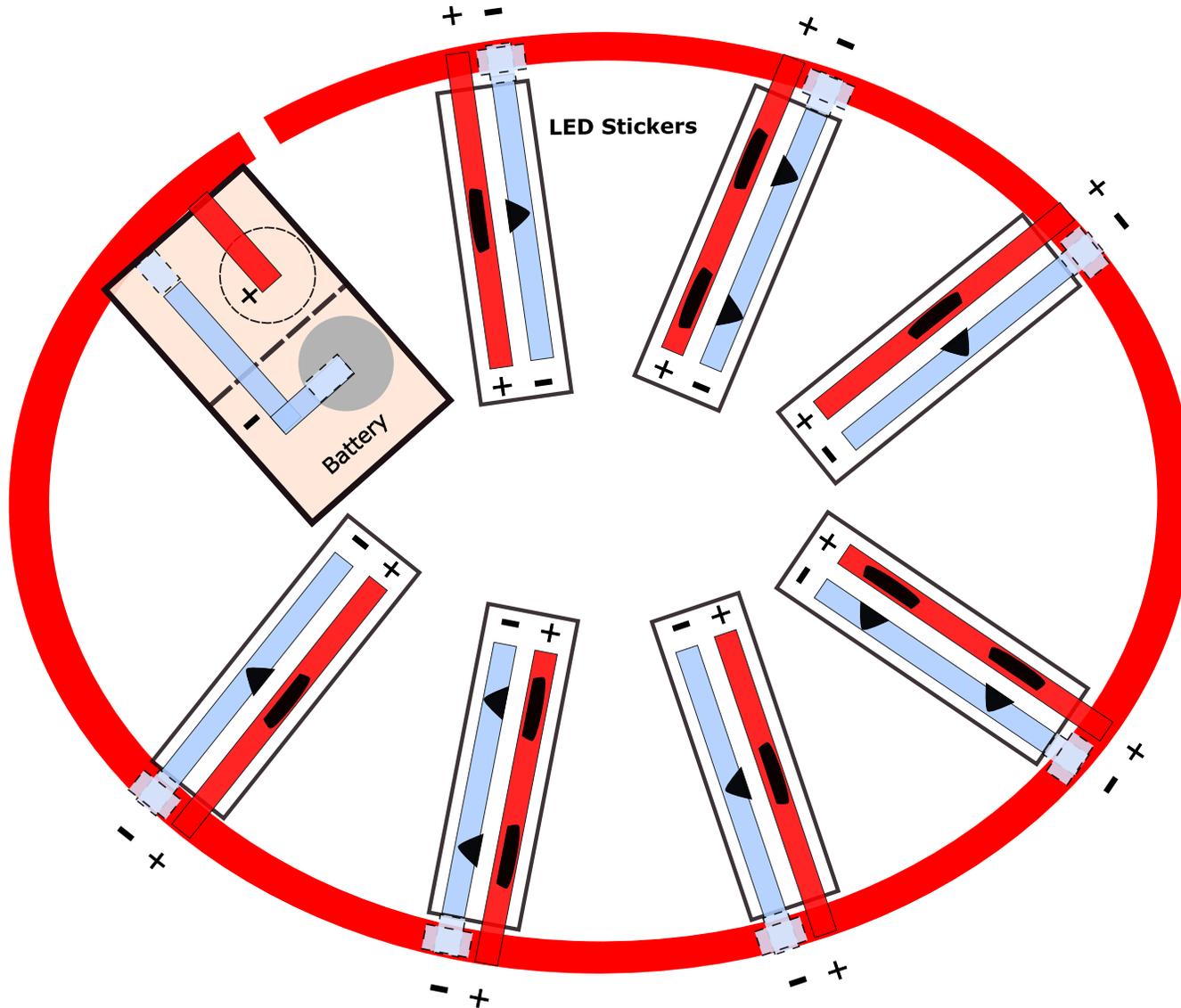


# Front View of Circuit

Not to scale



To create the power & ground rail for your Paper Circuit Chandelier, apply the positive lead to the front side of a 1/4" wide ribbon and the negative lead to the back side. You may add as many LED flags to your branching circuit as you wish.



Circuit Diagram for Paper Circuit Chandelier

@chibitronics

[www.chibitronics.com](http://www.chibitronics.com)

Created by Jill Dawson for Chibitronics

