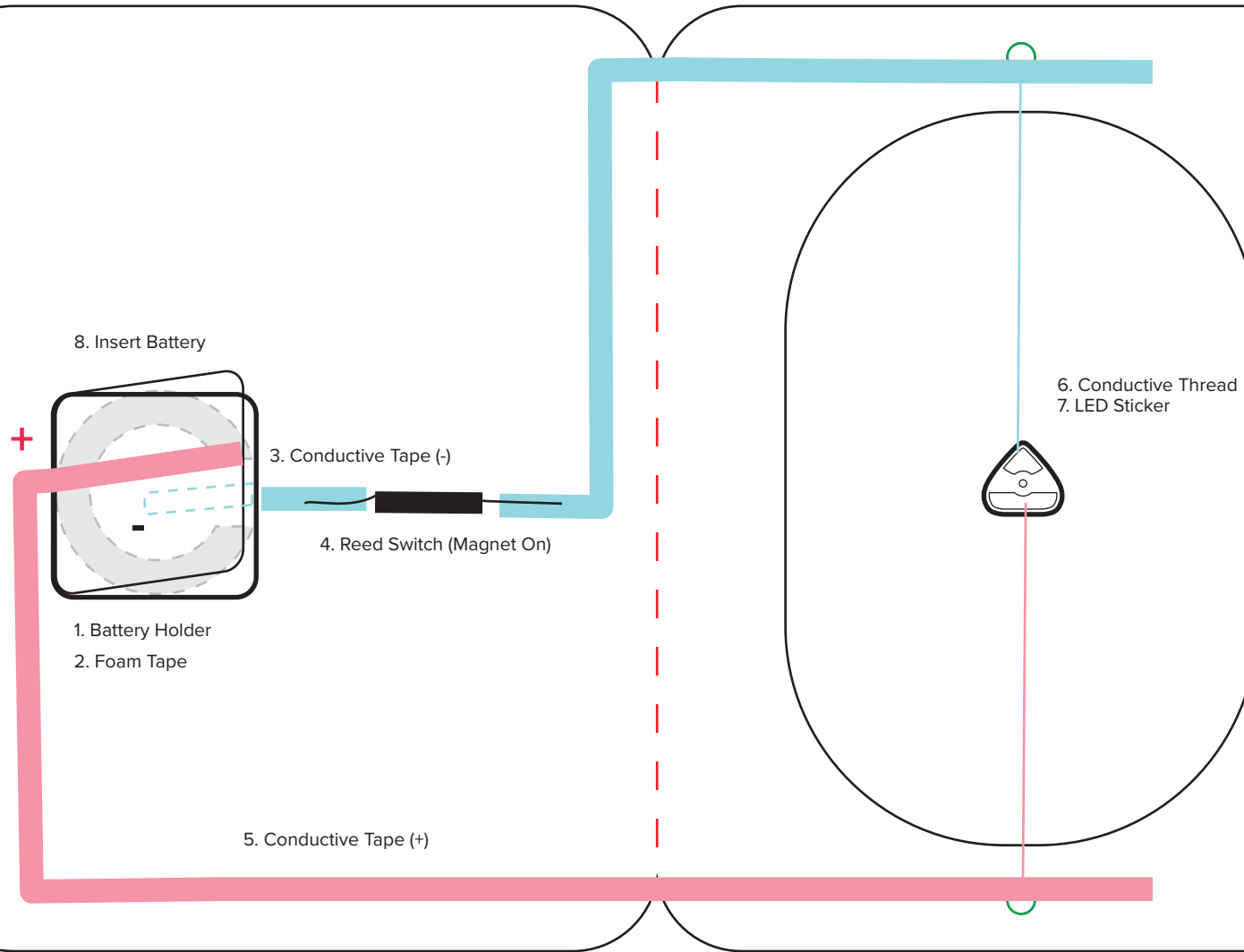


1 Inch



8. Insert Battery

+

3. Conductive Tape (-)

4. Reed Switch (Magnet On)

6. Conductive Thread  
7. LED Sticker

1. Battery Holder  
2. Foam Tape

5. Conductive Tape (+)



@chibitronics  
www.chibitronics.com

**Electricified Spinner Card**  
Created by Jill Dawson for Chibitronics

