
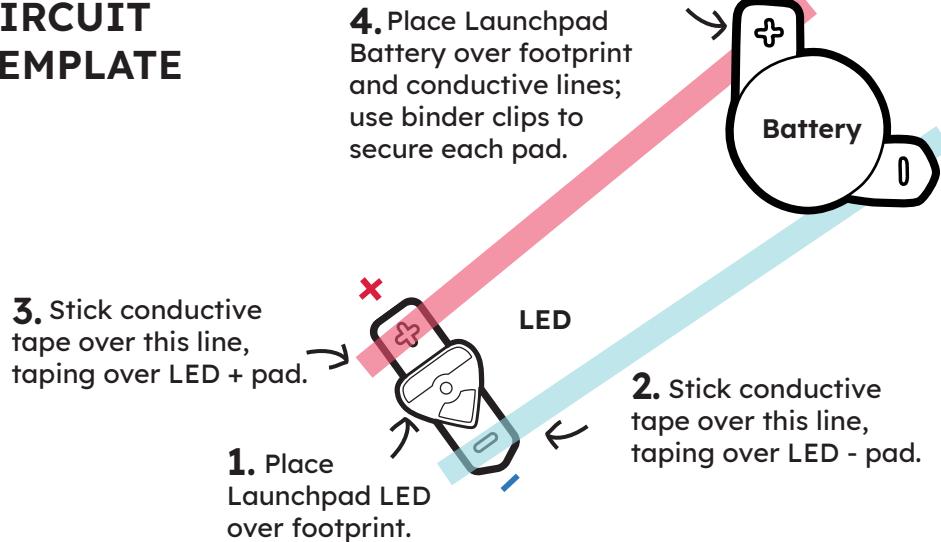


CIRCUIT TEMPLATE

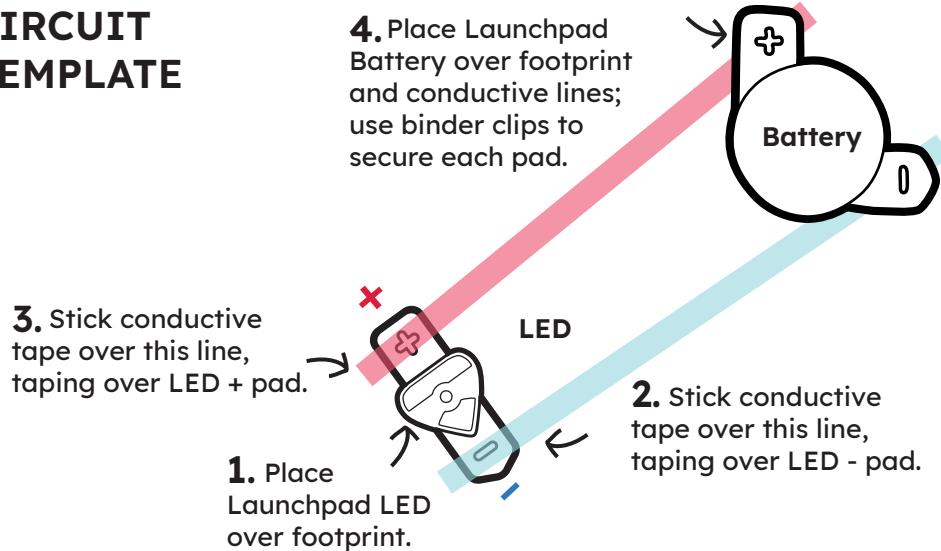

chibitronics.com 

CIRCUIT TEMPLATE




chibitronics.com 

Made with ❤ by:

Your Name

How does the circuit work?

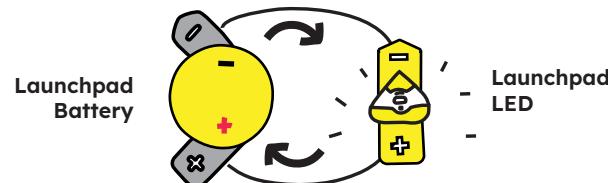When you connect the Launchpad LED the battery in a complete loop with conductive tape like this:



power from the battery flows through the LED light, causing it to shine. This continuous loop is called a complete circuit.

Check out chibitronics.com for more circuit crafting projects!




Made with ❤ by:

Your Name

How does the circuit work?

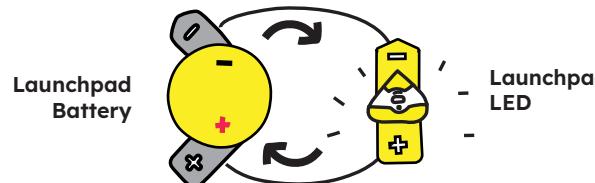When you connect the Launchpad LED the battery in a complete loop with conductive tape like this:



power from the battery flows through the LED light, causing it to shine. This continuous loop is called a complete circuit.

Check out chibitronics.com for more circuit crafting projects!

