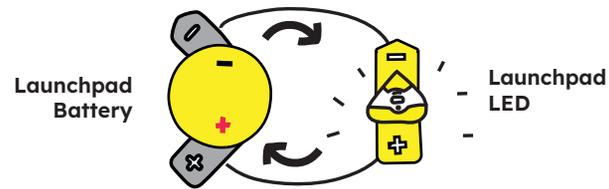


Made with ♥ by:

Your Name

How does the circuit work?

When you connect the Launchpad LED the battery in a complete loop with conductive tape like this:



power from the battery flows through the LED light, causing it to shine. This continuous loop is called a complete circuit.

Check out chibitronics.com for more circuit crafting projects!




Made with ♥ by:

Your Name

How does the circuit work?

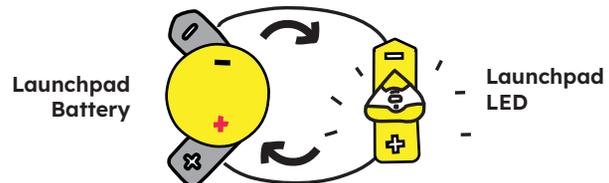When you connect the Launchpad LED the battery in a complete loop with conductive tape like this:



power from the battery flows through the LED light, causing it to shine. This continuous loop is called a complete circuit.

Check out chibitronics.com for more circuit crafting projects!



CIRCUIT TEMPLATE

3. Stick conductive tape over this line, taping over LED + pad.

1. Place Launchpad LED over footprint.

4. Place Launchpad Battery over footprint and conductive lines; use binder clips to secure each pad.

2. Stick conductive tape over this line, taping over LED - pad.



This work is licensed under a Creative Commons Attribution NonCommercial ShareAlike 4.0 International License.
<https://creativecommons.org/licenses/by-nc-sa/4.0/>

chibitronics.com



CIRCUIT TEMPLATE

3. Stick conductive tape over this line, taping over LED + pad.

1. Place Launchpad LED over footprint.

4. Place Launchpad Battery over footprint and conductive lines; use binder clips to secure each pad.

2. Stick conductive tape over this line, taping over LED - pad.



This work is licensed under a Creative Commons Attribution NonCommercial ShareAlike 4.0 International License.
<https://creativecommons.org/licenses/by-nc-sa/4.0/>

chibitronics.com

