


CIRCUIT TEMPLATE

4. Place Launchpad Battery over footprint and conductive lines; use binder clips to secure each pad.

1. Stick conductive tape over this line.

LED

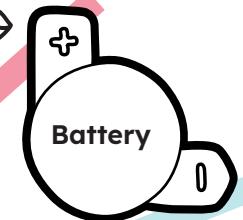3. Place Sticker LED over conductive tapes, aligned with footprint, and press firmly to ensure a strong connection.



2. Stick conductive tape over this line.

chibitronics.com



CIRCUIT TEMPLATE

4. Place Launchpad Battery over footprint and conductive lines; use binder clips to secure each pad.

1. Stick conductive tape over this line.

LED

3. Place Sticker LED over conductive tapes, aligned with footprint, and press firmly to ensure a strong connection.



2. Stick conductive tape over this line.

chibitronics.com




Made with ❤ by:

Your Name

How does the circuit work?

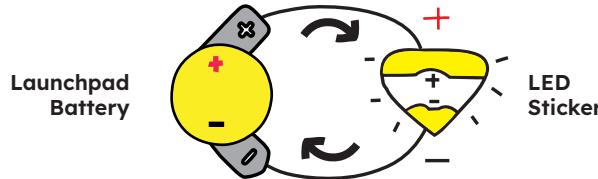When you connect the LED sticker to the battery in a complete loop with conductive tape like this:



power from the battery flows through the LED light, causing it to shine. This continuous loop is called a complete circuit.

Check out chibitronics.com for more circuit crafting projects!




Made with ❤ by:

Your Name

How does the circuit work?

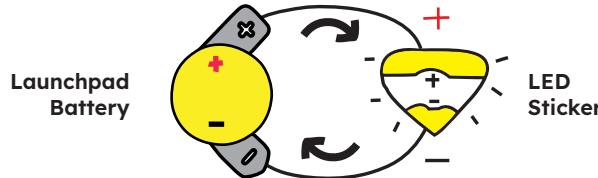When you connect the LED sticker to the battery in a complete loop with conductive tape like this:



power from the battery flows through the LED light, causing it to shine. This continuous loop is called a complete circuit.

Check out chibitronics.com for more circuit crafting projects!

